

ON Semiconductor

Is Now



To learn more about onsemi™, please visit our website at
www.onsemi.com

onsemi and onsemi. and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "onsemi" or its affiliates and/or subsidiaries in the United States and/or other countries. onsemi owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of onsemi product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. onsemi reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and onsemi makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does onsemi assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using onsemi products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by onsemi. "Typical" parameters which may be provided in onsemi data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. onsemi does not convey any license under any of its intellectual property rights nor the rights of others. onsemi products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use onsemi products for any such unintended or unauthorized application, Buyer shall indemnify and hold onsemi and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that onsemi was negligent regarding the design or manufacture of the part. onsemi is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.



ON Semiconductor®

<http://onsemi.com>

The CAT5132 Used for V_{COM} Buffer Control in a TFT LCD Display

Application Overview

All TFT (Thin-Film-Transistor) LCD panels require at least one appropriately tuned V_{COM} signal to provide a reference point for the panel's back plane (or back plate). Figure 1 is a simplified block diagram to provide the relationship of the V_{COM} inputs within an LCD panel with other inputs. The exact value of V_{COM} varies from panel to panel, so the manufacturer must program the voltage at the factory to match the characteristics of each screen. An appropriately tuned V_{COM} value reduces flicker and other undesirable effects.

Solution History

Traditionally, the V_{COM} adjustment made use of mechanical potentiometers or trimmers (see Figure 2) in the

APPLICATION NOTE

voltage-divider mode. In recent years, however, panel makers have begun looking at alternative approaches because inexpensive mechanical trimmers don't provide the manufacturing ease and desired reliability. The physical adjustment process on the assembly line also leads to inconsistent results from display to display. This adjustment is not only time-consuming, but also prone to field failures arising from human error and mechanical vibration. Additionally low cost mechanical potentiometers tended to be more vulnerable to environmental degradation over time causing long term reliability issues.

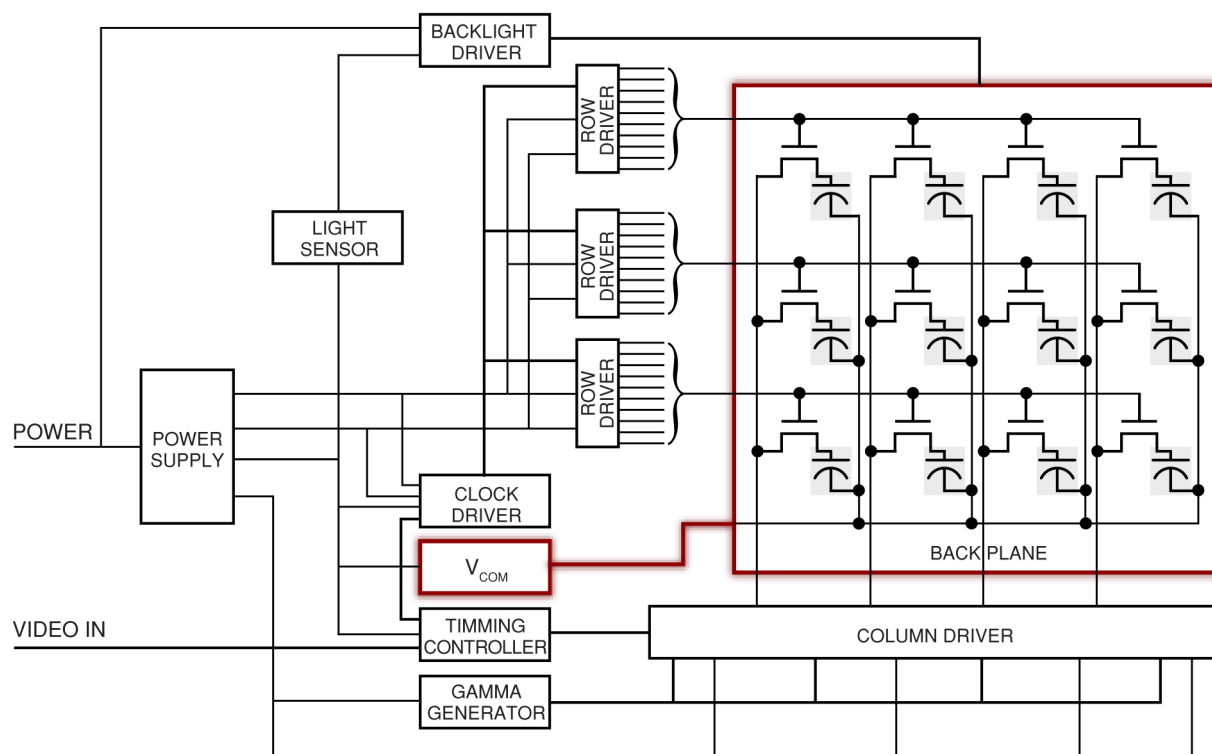


Figure 1. Simplified Block Diagram of a TFT LCD Display

The issues with the mechanical potentiometer solution lead vendors to seek an all silicon solution with the most obvious being to replace the mechanical potentiometer with a DAC as shown in Figure 3. This solution solved the problem of the degradation over time but was expensive. Not only did the DAC have to be very high resolution to deal with the fact that the DAC output was 0 V to 5 V and typically required a gain stage Op Amp in many circumstances to cover all the possible output ranges. Because DAC's are volatile they also required some form of direct control to set the output voltage after the display is powered on. This causes the system start up to be complex and time consuming.

The use of a nonvolatile digital potentiometer (POT) would address the issues with both of the above solutions. Because digital potentiometers have a serial bus input, they allow panel makers to automate the V_{COM} -adjustment process, resulting in lower manufacturing costs and higher product reliability. Additionally, since they are silicon devices like a DAC, they are not affected by typical

environmental issues and provide a very long life expectancy. Unlike a DAC however, using a resistive device with high voltage capabilities creates two additional advantages 1) a gross calibration can be achieved by the use of inexpensive external resistors putting the bits of resolution exactly where truly required, and 2) the high voltage capability removes the requirement for a gain stage Op Amp which reduces system noise.

The CAT5132 high voltage/nonvolatile digital potentiometer (Block Diagram shown in Figure 4) overcomes the complaints discussed above with mechanical potentiometers and DAC's. The CAT5132 is a 7 bit (128 position) all silicon potentiometer with a nonvolatile memory and capable of resistor terminal voltages as high as 16 V. The CAT5132 solution maintains the simplicity of the mechanical potentiometer solution while providing the versatility and reliability of the DAC solution at a much lower cost. Shown with a controller in Figure 5. The controller would only be required for the calibration process and would be omitted for normal operation.

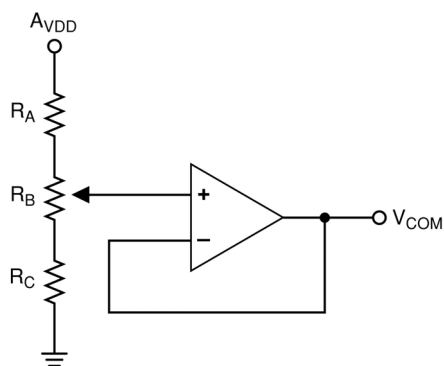


Figure 2. Typical Mechanical Potentiometer V_{COM} Solution with Op Amp in the Voltage Follower/Buffer configuration

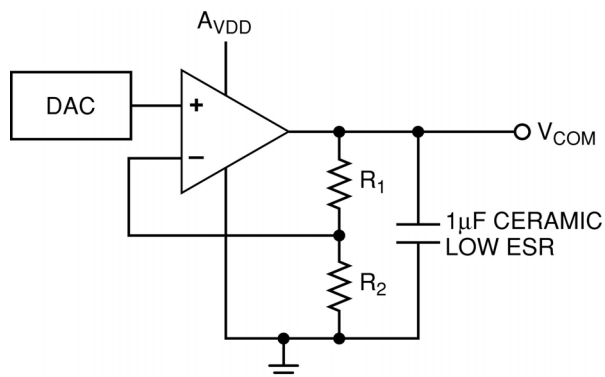


Figure 3. Typical DAC Implementation with an Op Amp Used as a Gain Stage/buffer

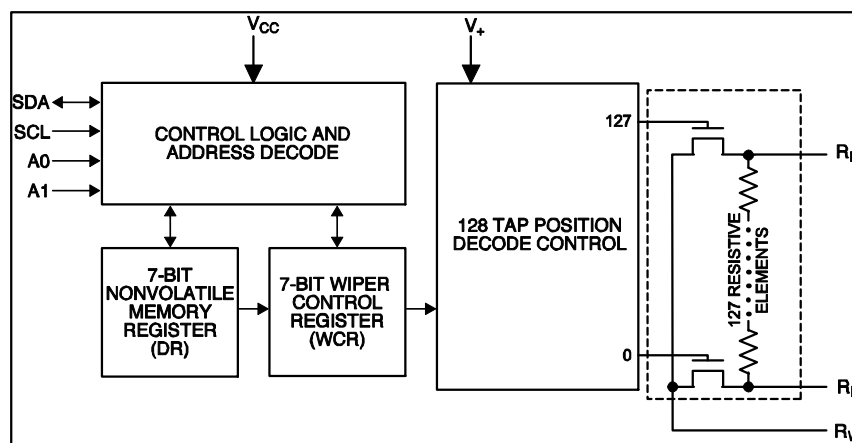


Figure 4. CAT5132 Block Diagram

The system implementation for a V_{COM} calibration with a CAT5132 is straightforward as shown in a typical application Figure 5. Resistors shown in Figure 5 (R1 and R3) can be adjusted to meet the specific needs of the display being adjusted but the basic circuit would be as shown. The Op Amp simply acts as a buffer for the variations in current required on the display back plane while the 1 μ F capacitor provides short duration current requirements. An I²C serial interface provides control and stores the desired potentiometer setting into the EEPROM. The 10 pin MSOP package also provides a small foot print to minimize space and removing the physical access for a manual adjustment can dramatically improve board layout efficiency for today's space-constrained designs.

Solution Implementation

The CAT5132 has a V_{CC} pin that is connected to any available logic supply. V_{CC} is 2.7 to 5.5 V and draws a maximum of 5 μ A except during a nonvolatile write when it can draw up to 3 mA. The analog input $V+$ draws a maximum of 10 μ A and is designed to be directly supplied from +8 to +16 V to bias the wiper switches in the digital

potentiometer's resistor string. If a panel requires a V_{COM} voltage greater than 16 V, the op amp could still be used in a non-inverting gain configuration however with a lower gain, noise will still be less than with an equivalent DAC solution.

The digital potentiometer has a maximum $\pm 20\%$ end-to-end resistor tolerance. The results in Table 1 show what could be expected using the circuit shown in Figure 5. It assumes that the tolerances of R1, R3, and V_{DD} are negligible compared with those of the potentiometer; you can expect the range of output values indicated. The desired value used for this example was V_{COM} at 7.2 V ± 0.5 V, with a step size of approximately 10 mV. The value R2 would be the value of the CAT5132 wiper to low potentiometer terminal minus the wiper resistance. The wiper resistance would have minimal impact in this voltage divider configuration driving a high impedance Op Amp input. And, despite the $\pm 20\%$ tolerance of R2, the midscale V_{COM} output meets the target specification. Also, because the digital potentiometer's logic supply matches the microcontroller's logic levels, the microcontroller can read the position data back if desired.

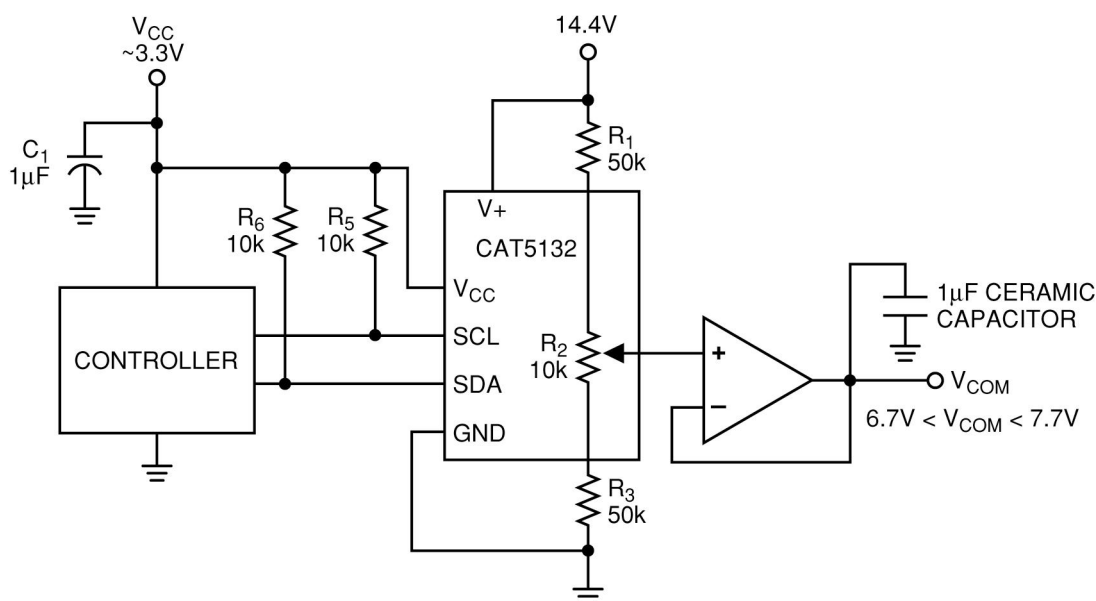


Figure 5. Typical Application Using the CAT5132

Table 1. OUTPUT VOLTAGE RANGE

R2 Tolerance, Scale	R2 (k Ω)	V_{COM} (V)	Step Size (mV)
-20%, Zero	0	6.65	8.3
-20%, Mid	4	7.18	
-20%, Full	8	7.71	
+20%, Zero	0	6.45	12.1
+20%, Mid	6	7.22	
+20%, Full	12	8.00	

NOTE: The value R2 used in this table is the value of the CAT5132 wiper to the low terminal minus the wiper resistance.

Calculations for Table 1:

Known Values:

Analog Voltage = 14.4 V

$R_1 + R_2 + R_3 = R_{\text{total}}$

Minimum Digital POT Resistance = 8 k Ω

Maximum Digital POT Resistance = 12 k Ω

External Resistors = 50 k Ω each

1. Determine total series resistance

Formula:

$R_1 + R_2 + R_3 = R_{\text{total}}$

Minimum Total Series Resistance:

$50 \text{ k}\Omega + 8 \text{ k}\Omega + 50 \text{ k}\Omega = 108 \text{ k}\Omega$

Maximum Total Series Resistance:

$50 \text{ k}\Omega + 12 \text{ k}\Omega + 50 \text{ k}\Omega = 112 \text{ k}\Omega$

2. Determine current through the resistive channel

Formula:

$\frac{\text{Analog Voltage}}{\text{Total Resistance}} = \text{Current}$

Minimum Resistance Current:

$\frac{14.4 \text{ V}}{108 \text{ k}\Omega} = 133 \mu\text{A}$

Maximum Resistance Current:

$\frac{14.4 \text{ V}}{112 \text{ k}\Omega} = 129 \mu\text{A}$

3. Determine Voltages at the output of the Digital POT

Formula:

$\text{Current} * \text{Resistance} = \text{Voltage}$

Minimum Digital POT Resistance Calculations @ Wiper output:

Minimum Voltage:

$133 \mu\text{A} * 50 \text{ k}\Omega = 6.65 \text{ V}$

Middle Voltage:

$133 \mu\text{A} * 54 \text{ k}\Omega + 7.18 \text{ V}$

Maximum Voltage:

$133 \mu\text{A} * 58 \text{ k}\Omega + 7.71 \text{ V}$

Maximum Digital POT Resistance Calculations @ Wiper output:

Minimum Voltage:

$129 \mu\text{A} * 50 \text{ k}\Omega = 6.45 \text{ V}$

Middle Voltage:

$129 \mu\text{A} * 56 \text{ k}\Omega + 7.22 \text{ V}$

Maximum Voltage:

$129 \mu\text{A} * 62 \text{ k}\Omega + 8.00 \text{ V}$

4. Determine LSB step voltage

Formula:


$\frac{V_{\text{FULL}} - V_{\text{Zero}}}{\# \text{ of Steps}} = \text{Voltage Step}$

Step Size Digital POT Minimum Resistance:

$\frac{7.71 \text{ V} - 6.65 \text{ V}}{128} = 8.3 \text{ mV}$

Step Size Digital POT Maximum Resistance:

$\frac{8.00 \text{ V} - 6.45 \text{ V}}{128} = 12.1 \text{ mV}$

ON Semiconductor and  are registered trademarks of Semiconductor Components Industries, LLC (SCILLC). SCILLC owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of SCILLC's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. SCILLC reserves the right to make changes without further notice to any products herein. SCILLC makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does SCILLC assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. "Typical" parameters which may be provided in SCILLC data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. SCILLC does not convey any license under its patent rights nor the rights of others. SCILLC products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the SCILLC product could create a situation where personal injury or death may occur. Should Buyer purchase or use SCILLC products for any such unintended or unauthorized application, Buyer shall indemnify and hold SCILLC and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that SCILLC was negligent regarding the design or manufacture of the part. SCILLC is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor
P.O. Box 5163, Denver, Colorado 80217 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
USA/Canada

Europe, Middle East and Africa Technical Support:
Phone: 421 33 790 2910

Japan Customer Focus Center
Phone: 81-3-5817-1050

ON Semiconductor Website: www.onsemi.com

Order Literature: <http://www.onsemi.com/orderlit>

For additional information, please contact your local
Sales Representative