



Is Now Part of



**ON Semiconductor®**

To learn more about ON Semiconductor, please visit our website at  
[www.onsemi.com](http://www.onsemi.com)

ON Semiconductor and the ON Semiconductor logo are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

# AN-6606

## Simple VHF Analog Switches

Simple JFET switches like those in Figure 1 will toggle at rates to about 10 MHz and switch analog signals with frequencies to above 100 MHz. They accomplish this by resolving in the gate-driver design the contradictory performance goals that even the best switching transistors cannot meet.

To switch high-frequency signals, the JFET should have low ON impedance,  $r_{ds(on)}$  or  $R_{ON}$ , and low input capacitance,  $C_{iss}$ . The switch's RC time constant is established by these 2 parameters, and they also indicate the bandwidth capability. JFETs have been developed that come close to being ideal, but unfortunately the real-world nature of semiconductor devices makes it impossible to achieve optimum values of both parameters in the same device. Low  $R_{ON}$  calls for a physically large JFET. On the other hand, the very low capacitance needed for fast toggle rates implies small size.

At a casual glance, gate drive impedance does not appear very important. However, the JFET device conflict between  $R_{ON}$  and  $C_{iss}$  may be overcome by using the proper gate driver. The drive circuit should have low impedance when the JFET is turned OFF and high impedance when the JFET is turned ON. The low-impedance path is needed to prevent analog-signal feed-through and the high impedance to minimize signal attenuation through the driver while the JFET is conducting. A well-designed driver can do both.

The relationships among JFET and driver characteristics can be sorted out with the help of Figure 2, which shows a typical series-pass switch and the equivalent circuits of the JFET in its ON and OFF conditions. A JFET operates best as a series-pass switch when the ON condition allows  $R_{ON}$  and shunt capacitance to be low, and series-pass capacitance to be high. But in the OFF condition, it should exhibit low series-pass capacitance and high series-pass resistance ( $R_{OFF}$ ). The JFET will have these characteristics when properly matched to the driver.



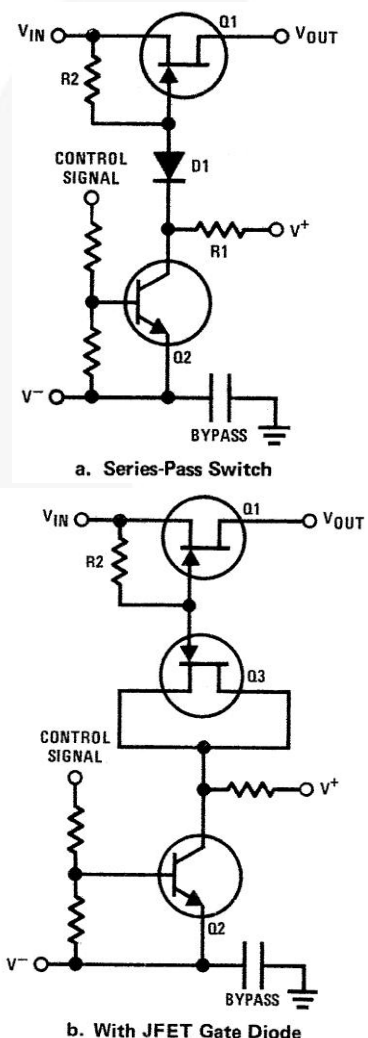



Figure 1. High-Frequency JFET Switching Circuits

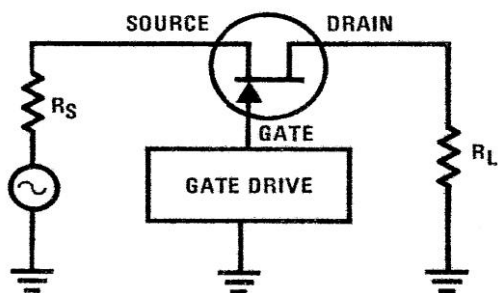

a. Series-Pass JFET Switch

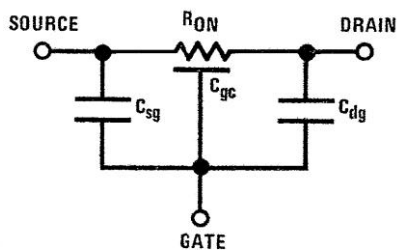

b. JFET On

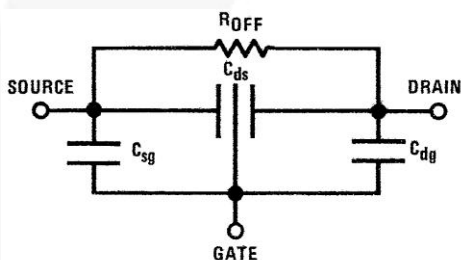

c. JFET Off

- $C_{dg}$  = drain-gate capacitance
- $C_{gc}$  = gate-channel distributed capacitance
- $C_{sg}$  = source-gate capacitance
- $C_{ds}$  = drain-source capacitance
- $R_{ON}$  = ON impedance
- $R_{OFF}$  = OFF impedance

**Figure 2. Series Pass Switch and JFET Equivalent Circuits**

Getting down to a low  $R_{ON}$  when the gate is turned ON is no problem. A JFET such as the 2N4391 has a maximum  $R_{ON}$  of 30 ohms (see  $r_{ds(on)}$  in Table 1). However, the parallel capacitance in the signal path can become fairly high - about 15 pF when drain, source and gate have the same potential ( $V_{DS} = V_{GS} = 0$ ). The simple answer to this dilemma is to drive the gate with high AC impedance when the switch is closed. The shunt capacitance will be in series with high impedance. Virtually all of the signal will then go through the JFET, the path of least resistance, rather than through the gate-to-ground connection.

Next problem; when the switch is OFF, high-frequency attenuation is the name of the game. It is depended upon to prevent the signal at the input from reaching the output. The JFET channel is, for all practical purposes, an open circuit because  $R_{OFF}$  of a quality JFET is over  $10^{12}$  ohms although this decreases as frequency goes up. However, capacitive feed-through is the most significant route across the switch. From Figure 2c.

$$C_{FEEDTHROUGH} = C_{ds} + \frac{C_{sg}C_{dg}}{C_{sg} + C_{dg}}$$

Feed-through capacitance can be significant if the gate is not operated at AC ground. Minimizing the right-hand term by operating the gate at AC ground allows  $C_{ds}$  to become the pacing factor. If the gate is grounded,  $C_{ds}$  will be approximately 0.2 pF. In other words, the effective  $R_{OFF}$  of the switch depends directly on circuit design, not the JFET.

Now to put these principles to work; the best high-frequency switch is an N-channel JFET. Its gate should be biased positive from a high-impedance source for turn-on and biased negative through a low-impedance path for turn-off. Driving the switch ON through an RF choke sounds tempting, but it would be difficult to avoid resonances and oscillation bursts during some switching conditions. DC resistances could be increased to equal or exceed  $R_S$  in parallel with  $R_L$ , but then the toggle rate would be kept down by the very high drive impedance.

We prefer the circuits in Figure 1, which are fairly fast and not tricky. When NPN transistor Q2 is in saturation, Q1 is biased OFF through a low-impedance path. The diode is slightly forward-biased and exhibits high capacitance. When Q2 turns OFF, D1's cathode is driven positive by R1. Now the diode is reverse-biased and exhibits high impedance and low capacitance. The charge that was stored on D1 discharges into the gate of Q1, allowing the JFET to be turned ON. Because there is no good discharge path available to the charge stored on Q1's gate, the gate will "follow" any signal swing in the analog input voltage. Adding R2 will ensure that the gate follows the signal even during DC conditions. Remember, however, that the  $R2/C_{sg}$  time constant will effect switching time and gate-source signal tracking.

Don't expect just any diode to work well; D1's capacitance is critical and should match that of the JFET ( $C_{D1} = C_{Q1}$ ). One good way of making sure that the JFET and the diode are well mated is to use the same type of JFET for both. The gate lead is one electrode of the diode and the drain and source leads are simply tied together to form the other electrode. The circuit in Figure 1b was optimized in this way.

Excellent high-frequency series switches can be made with 2N4091, 2N4092 and 2N4093 JFETs. RC time constants are short because of their low  $r_{ds(on)}$  and capacitance, and leakage is low. The 2N4391, 2N4392 and 2N4393 series is even better, having only 100 pA leakage and lower  $C_{iss}$ . Even though the 2N4416 is classed as an RF amplifier, it is also listed in Table (1) to illustrate that many of our other JFETs can solve special switching problems. This one does well in circuits

requiring very low capacitance and leakage. Although the  $R_{ON}$  of an RF transistor is not specified, it can be estimated as  $r_{ds(on)} \approx 0.85/Yfs$ , which is typically 170 ohm for the 2N4416.



TABLE I. JFETs for High-Frequency Analog Signal Switching

TYPE NO.	$BV_{GSS}$ OR $BV_{DGO}$ (MAX)	$I_{GSS}$ (MAX)	$C_{iss}$ (MAX)	$C_{rss}$ OR $C_{DGO}$ (MAX)	$r_{ds(on)}$ (MAX)	$t_{on}$ (MAX)	$t_{off}$ (MAX)
2N4091	40V	0.2 nA	16 pF	5 pF	30 $\Omega$	25 ns	40 ns
2N4092	40V	0.2 nA	16 pF	5 pF	50 $\Omega$	35 ns	60 ns
2N4093	40V	0.2 nA	16 pF	5 pF	80 $\Omega$	60 ns	80 ns
2N4391	40V	0.1 nA	14 pF	3.5 pF	30 $\Omega$	15 ns	20 ns
2N4392	40V	0.1 nA	14 pF	3.5 pF	60 $\Omega$	15 ns	35 ns
2N4393	40V	0.1 nA	14 pF	3.5 pF	100 $\Omega$	15 ns	50 ns
2N4416	30V	0.1 nA	4 pF	0.8 pF	170 $\Omega$ *		
2N4416A	35V	0.1 nA	4 pF	0.8 pF	170 $\Omega$ *		

\*This value is not specified in RF amplifier JFETs; 170 $\Omega$  is typical

Author: Mike Turner, Feb 1977, FET Brief 1

#### DISCLAIMER

FAIRCHILD SEMICONDUCTOR RESERVES THE RIGHT TO MAKE CHANGES WITHOUT FURTHER NOTICE TO ANY PRODUCTS HEREIN TO IMPROVE RELIABILITY, FUNCTION, OR DESIGN. FAIRCHILD DOES NOT ASSUME ANY LIABILITY ARISING OUT OF THE APPLICATION OR USE OF ANY PRODUCT OR CIRCUIT DESCRIBED HEREIN; NEITHER DOES IT CONVEY ANY LICENSE UNDER ITS PATENT RIGHTS, NOR THE RIGHTS OF OTHERS.

#### LIFE SUPPORT POLICY

FAIRCHILD'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF FAIRCHILD SEMICONDUCTOR CORPORATION.

As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, or (c) whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

ON Semiconductor and  are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

## PUBLICATION ORDERING INFORMATION

### LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor  
19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA  
**Phone:** 303-675-2175 or 800-344-3860 Toll Free USA/Canada  
**Fax:** 303-675-2176 or 800-344-3867 Toll Free USA/Canada  
**Email:** [orderlit@onsemi.com](mailto:orderlit@onsemi.com)

**N. American Technical Support:** 800-282-9855 Toll Free  
USA/Canada  
**Europe, Middle East and Africa Technical Support:**  
Phone: 421 33 790 2910  
**Japan Customer Focus Center**  
Phone: 81-3-5817-1050

**ON Semiconductor Website:** [www.onsemi.com](http://www.onsemi.com)  
**Order Literature:** <http://www.onsemi.com/orderlit>  
For additional information, please contact your local  
Sales Representative