



Is Now Part of



**ON Semiconductor®**

To learn more about ON Semiconductor, please visit our website at  
[www.onsemi.com](http://www.onsemi.com)

ON Semiconductor and the ON Semiconductor logo are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

# AN-8211

## Designing for High Performance Commercial and Industrial Lighting Solution Using FL77905 Compact Dimmable LED Direct AC Driver

### Introduction

The FL77905 is a LED Direct AC driver. It integrates three constant current regulators, which can withstand up to 500 V on LED1 and LED2 pin and 200 V on LED3 pin. FL77905 is the ideal solution for driving string of series connected LEDs directly from the rectified AC line voltage of 80~305 V<sub>AC</sub> with analog or Pulse-Width-Modulated (PWM) dimming input. This application note provides practical guidelines for designing high performance commercial and industrial lighting solutions using FL77905.

### Operation

Figure 1 shows the internal block diagram of FL77905 and Figure 2 shows its principle of operation. FL77905 controls the LED's current to be in phase with the rectified AC line voltage via three constant-current regulators within the IC. The LED currents that flow through each of the internal current regulator,  $I_{LED1} \sim I_{LED3}$ , are set by an external current sensing resistor ( $R_{CS}$ ). The regulated current level through each channel as well as the total Root-Mean-Square (RMS) input current can be calculated as follow.

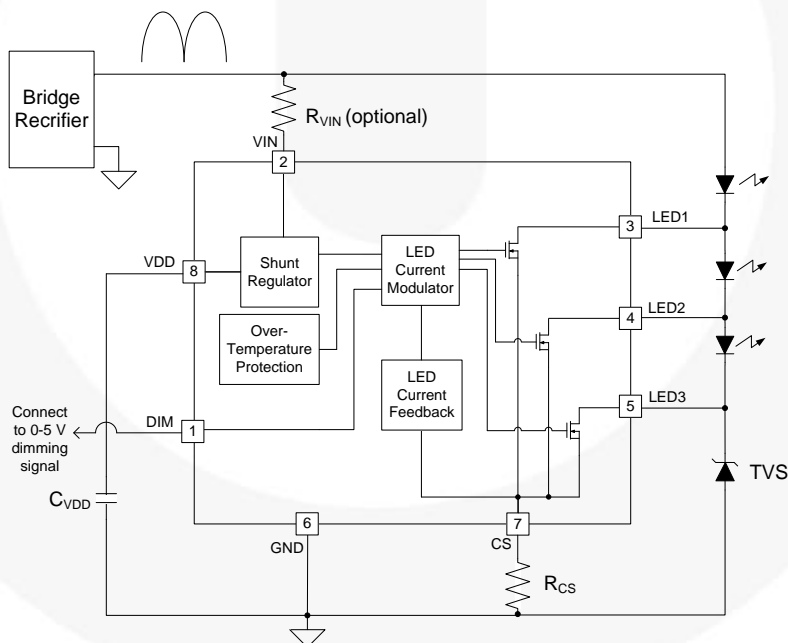


Figure 1. FL77905 Block Diagram

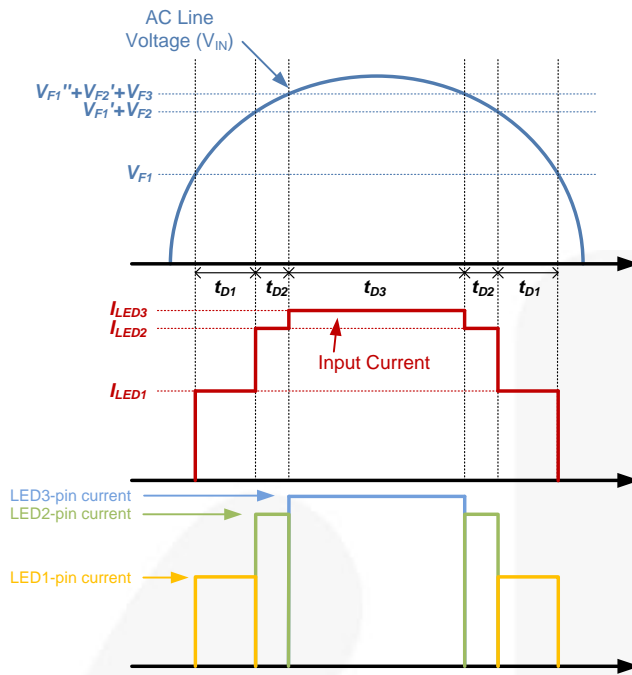


Figure 2. Drawing of Principle Operating Waveform

- $t_{D1}$ : Current is directed to LED1 pin through 1<sup>st</sup> LED group.
- $t_{D2}$ : Current is directed to LED2 pin through 1<sup>st</sup> and 2<sup>nd</sup> LED groups.
- $t_{D3}$ : Current is directed to LED3 pin through 1<sup>st</sup>, 2<sup>nd</sup>, and 3<sup>rd</sup> LED groups.
- $V_{F1}/V_{F1}'/V_{F1}''$ : Forward voltage at forward current of  $I_{LED1}/I_{LED2}/I_{LED3}$  in 1<sup>st</sup> LED group.
- $V_{F2}/V_{F2}'$ : Forward voltage at forward current of  $I_{LED2}/I_{LED3}$  in 2<sup>nd</sup> LED group.
- $V_{F3}$ : Forward voltage at forward current of  $I_{LED3}$  in 3<sup>rd</sup> LED group.

$$I_{LED1} = \frac{0.47}{R_{CS}} \quad (1)$$

$$I_{LED2} = \frac{0.86}{R_{CS}} \quad (2)$$

$$I_{LED3} = \frac{0.96}{R_{CS}} \quad (3)$$

$$I_{IN,RMS} = \frac{0.96}{1.3 \times R_{CS}} \quad (4)$$


$$R_{CS} = \frac{0.96 \times V_{AC,RMS}}{1.3 \times P_{IN}} \quad (5)$$

The number “1.3” in equation (4) and (5) is the AC input current crest factor which depends on the LED configuration. It is normally 1.3 for FL77905 when LEDs are configured to have identical forward voltages in each group.  $V_{AC,RMS}$  is the RMS value of the AC input voltage, and  $P_{IN}$  is the input power. For different LED configuration, crest factor can be in the range of 1.3 to 1.6. In that case, fine tuning on  $R_{CS}$  value is required to have precise targeted  $P_{IN}$ .

When the rectified AC line voltage  $V_{IN}$ , reaches a certain level, the internal reference and shunt regulator of the FL77905 starts to power up the IC's internal circuits. At this point, all the internal constant current regulators are ready to sink LED current as soon as there is sufficient voltage across the input to forward bias the LED string and maintain enough voltage headroom at the corresponding LED channel. As  $V_{IN}$  increases, current in the current regulator increases linearly to the predefined level and is maintained at that level until there is sufficient  $V_{IN}$  to forward bias the next group of LEDs.

For example, at the start of  $t_{D1}$  in Figure 2,  $V_{IN}$  reaches the forward voltage across the 1st group of LEDs ( $V_{F1}$ ) at the forward current ( $I_F$ ) equal to  $I_{LED1}$ ,  $I_{LED1}$  is now drawn from the input and directed into pin LED1 through the 1st group of LED. As the input voltage increases and  $V_{IN}$  reaches the total forward voltage across the 1st and 2nd group of LED ( $V_{F1}' + V_{F2}$ ) at  $I_F = I_{LED2}$ ,  $I_{LED2}$  is then directed into pin LED2 through the 1st group and 2nd group of LEDs. Finally, when  $V_{IN}$  reaches  $V_{F1}'' + V_{F2}' + V_{F3}$ , which are the forward voltages for the respective group of LEDs at  $I_F = I_{LED3}$ ,  $I_{LED3}$  then goes through the 1st, 2nd, and 3rd group of LEDs and into pin LED3.

As the  $V_{IN}$  varies and the active channel (the one that is sinking LED current) commutates from one channel to the adjacent channel, current in the new active channel increases gradually while current in the previously conducting channel decreases. Figure 2 shows the current transitions described above, but it does not show the linear behavior of increase and decrease of the currents. Figure 3 shows the input waveforms based on a 7.5-W design.

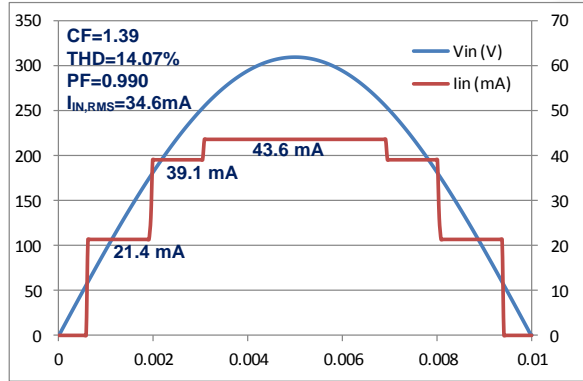

**Figure 3. Input Voltage and Current (7.5 W Input Power,  $R_{CS}=22 \Omega$  at AC 220 V)**

## LED Current Approximation

The RMS LED current is managed by an external LED current setting resistor,  $R_{CS}$ , and each LED channel current level depends on the  $R_{CS}$  value. Assuming that the LED current into the LED channels are rectangular pulses, the RMS LED current can be calculated using the procedure below.

The peak value of rectified AC line voltage is:

$$V_{IN,PEAK} = \sqrt{2} \cdot V_{AC,RMS} - V_D \quad (6)$$

where  $V_D$  is the forward voltage drop across input bridge rectifier diodes.

The length of time during which each of the FL77905's internal current regulator will conduct over the AC line's half cycle can be calculated through calculating  $T_1$ ,  $T_2$ , and  $T_3$  in Figure 4.

$$T_1 = \sin^{-1} \left[ \frac{V_{F1}}{V_{IN,PEAK}} \right] \cdot \frac{1}{2\pi \cdot f_{AC}} \quad (7)$$

$$T_2 = \sin^{-1} \left[ \frac{V_{F1}' + V_{F2}}{V_{IN,PEAK}} \right] \cdot \frac{1}{2\pi \cdot f_{AC}} \quad (8)$$

$$T_3 = \sin^{-1} \left[ \frac{V_{F1}'' + V_{F2}' + V_{F3}}{V_{IN,PEAK}} \right] \cdot \frac{1}{2\pi \cdot f_{AC}} \quad (9)$$

where

- $f_{AC}$  = AC line frequency
- $V_{F1}/V_{F1}'/V_{F1}''$  = Forward voltage at forward current of  $I_{LED1}/I_{LED2}/I_{LED3}$  in the 1st LED group.
- $V_{F2}/V_{F2}'$  = Forward voltage at forward current of  $I_{LED2}/I_{LED3}$  in the 2nd LED group.
- $V_{F3}$  = Forward voltage at forward current of  $I_{LED3}$  in the 3<sup>rd</sup> LED group.

The RMS current of each LED channel can be calculated as follows:

$$I_{LED1,RMS} = I_{LED1} \cdot \sqrt{4 \cdot f_{AC} \cdot (T_2 - T_1)} \quad (10)$$

$$I_{LED2,RMS} = I_{LED2} \cdot \sqrt{4 \cdot f_{AC} \cdot (T_3 - T_2)} \quad (11)$$

$$I_{LED3,RMS} = I_{LED3} \cdot \sqrt{1 - 4 \cdot f_{AC} \cdot T_3} \quad (12)$$

- $I_{LED1,RMS}$  = RMS current sunk to LED1 channel
- $I_{LED2,RMS}$  = RMS current sunk to LED2 channel
- $I_{LED3,RMS}$  = RMS current sunk to LED3 channel


The RMS current that flows through each LED group and RMS value of input current can be obtained as follows:

$$I_{F1,RMS} = I_{IN,RMS} = \sqrt{I_{LED1,RMS}^2 + I_{LED2,RMS}^2 + I_{LED3,RMS}^2} \quad (13)$$

$$I_{F2,RMS} = \sqrt{I_{LED2,RMS}^2 + I_{LED3,RMS}^2} \quad (14)$$

$$I_{F3,RMS} = I_{LED3,RMS} \quad (15)$$

- $I_{F1,RMS}$  = RMS current flowed through 1<sup>st</sup> LED group
- $I_{F2,RMS}$  = RMS current flowed through 2<sup>nd</sup> LED group
- $I_{F3,RMS}$  = RMS current flowed through 3<sup>rd</sup> LED group

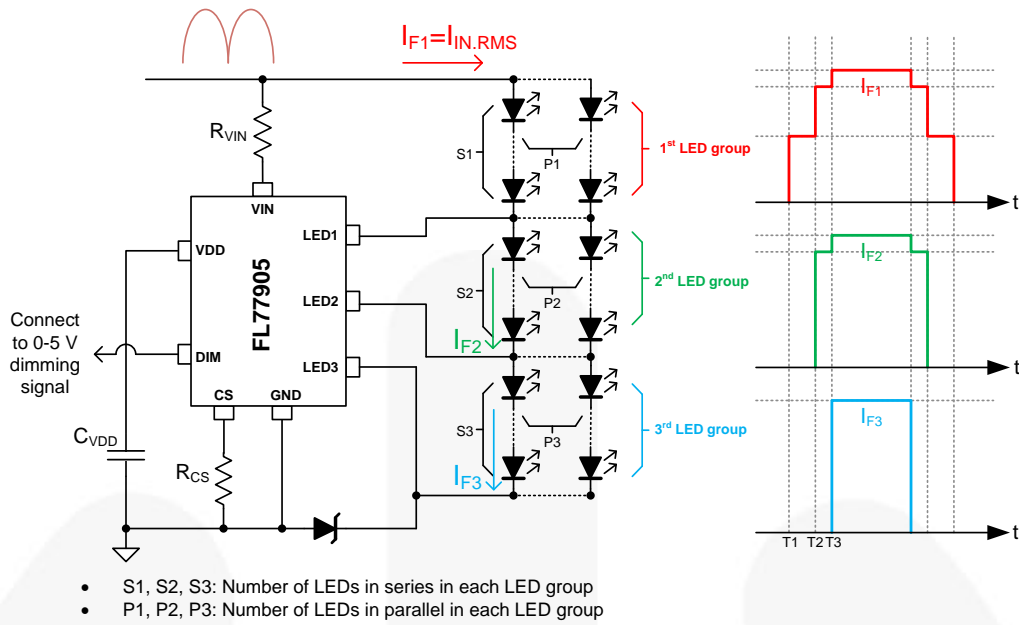

**Figure 4. LED Current for Each LED Group During a Half Cycle of the AC Line**

Besides RMS values, the average values of currents in LED1~4 pins can also be calculated.

$$I_{LED1,AVG} = I_{LED1} \cdot 4 \cdot f_{AC} \cdot (T_2 - T_1) \quad (16)$$

$$I_{LED2,AVG} = I_{LED2} \cdot 4 \cdot f_{AC} \cdot (T_3 - T_2) \quad (17)$$

$$I_{LED3,AVG} = I_{LED3} \cdot (1 - 4 \cdot f_{AC} \cdot T_3) \quad (18)$$

- $I_{LED1,AVG}$  = average current sunk to LED1 channel
- $I_{LED2,AVG}$  = average current sunk to LED2 channel
- $I_{LED3,AVG}$  = average current sunk to LED3 channel

The average current information can be used to estimate power that is consumed in each LED. Power on each LED group can be calculated as follows:

$$P_{F1} = I_{LED1,AVG} \cdot V_{F1} + I_{LED2,AVG} \cdot V_{F1}' + I_{LED3,AVG} \cdot V_{F1}'' \quad (19)$$

$$P_{F2} = I_{LED2,AVG} \cdot V_{F2} + I_{LED3,AVG} \cdot V_{F2}' \quad (20)$$

$$P_{F3} = I_{LED3,AVG} \cdot V_{F3} \quad (21)$$

$P_{F1}$  = Power consumed on 1<sup>st</sup> LED group

- $P_{F2}$  = Power consumed on 2<sup>nd</sup> LED group
- $P_{F3}$  = Power consumed on 3<sup>rd</sup> LED group

Luminous flux of LED is approximately proportional to its forward current. The average current flow through each LED group can be obtained as follows.

$$I_{F1,AVG} = I_{LED1,AVG} + I_{LED2,AVG} + I_{LED3,AVG} \quad (22)$$

$$I_{F2,AVG} = I_{LED2,AVG} + I_{LED3,AVG} \quad (23)$$

$$I_{F3,AVG} = I_{LED3,AVG} \quad (24)$$

- $I_{F1,AVG}$  = average current flowed through 1<sup>st</sup> LED group

- $I_{F2,AVG}$  = average current flowed through 2<sup>nd</sup> LED group
- $I_{F3,AVG}$  = average current flowed through 3<sup>rd</sup> LED group

## Design LED Configuration

Referring to Figure 4, LEDs driven by FL77905 are arranged as three groups. Each group has its series quantity (S1~S3) and parallel quantity (P1~P3). Key point of a design process is to decide these quantities.

To decide S1~S3, the total forward-drop voltage ( $V_F$ ) across the series connected groups of LEDs is the key design consideration. A good starting point is 1.2 times of RMS value of the input voltage. For example, a design may have approximately 250 V~270 V of total  $V_F$  for 220 V<sub>AC</sub> input and 130 V~140 V of total  $V_F$  for 120 V<sub>AC</sub> input.  $V_F$  across each LED group can be adjusted for performance tuning while keeping the same total  $V_F$ . As the total  $V_F$  increases, efficiency goes up and Total Harmonic Distortion (THD) improves, but line regulation becomes worse. If the total  $V_F$  decreases, line regulation becomes better but efficiency decreases.


P1~P3 is basically decided by current rating and power rating of the LEDs. With a fixed  $R_{CS}$  value, peak current flowing through each LED group can be got from equation (3), and average current in each LED group can be calculated from equation (22)~(24). Start with using just rated forward voltage multiplied by pre-decided S1~S4 in the equations, how many LEDs need be put in parallel can be estimated.

When all these quantities are decided, going through the equations as the helps confirming if the design target can be met. Refer to [AN-5088](#) [1] for guidance of surge compatibility, and PCB layout considerations.

## Compact-Size Design

The total  $V_F$  needs to be about 260 V at 220 V<sub>AC</sub> and 130 V at AC 120 V<sub>AC</sub>. Assuming  $P_1=P_2=P_3=1$ , minimum LED quantity is  $S_1+S_2+S_3$ , which can be got from dividing total  $V_F$  by  $V_F$  of a single LED. For compact size, as quantity of

LEDs might be limited, high- $V_F$  LEDs are recommended. As shown in Figure 5, each LED has 65 V of  $V_F$ . If conventional low-voltage LEDs are used, such as 0.06 W LEDs ( $V_F=3$  V,  $I_F=20$  mA) or 0.2 W LEDs ( $V_F=3$  V,  $I_F=65$  mA), a long LED array is needed, which may not be acceptable since it takes too much of PCB real estate.

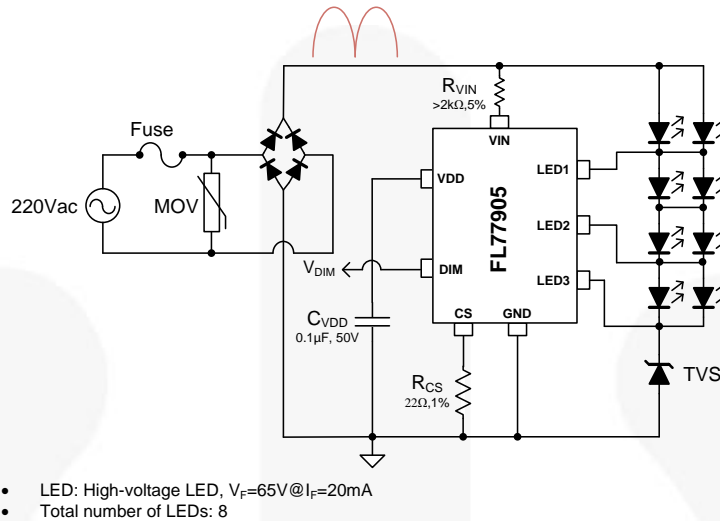

**Figure 5. 220-V<sub>AC</sub> 7.5-W Down Light Design for Commercial Lighting Application using 65-V<sub>F</sub> LEDs**

## Long-String LED Design


When conventional low-voltage LED are implemented in a direct AC driving system, a long LED string will be presented in the schematic. It is optimum for designs requiring LEDs to be spread to larger area.

An example is tube-type design. Tube type LED lighting design requires tight balancing of light output at each part of the tube. FL77905 sequentially turns on each LED group thus current imbalance is inevitable. Possible ways to reduce the current imbalance are discussed below.


- Use different number of parallel LED string for each of the LED groups. For example, 1<sup>st</sup> LED group has the highest current and 3<sup>rd</sup> LED group has the lowest current, so the 1<sup>st</sup> LED group will have the most number of parallel LED strings and 3<sup>rd</sup> LED group will

have the least number of parallel LED strings, as shown in Figure 6

- Use different spacing between different LED groups based on their average current, as shown in Figure 7.
- Spread LEDs of each group evenly throughout the area. For example, if it's chosen to use 3X parallel LEDs (such as 5050 LED) in one package and have equal lighting distribution across light fixture, it is recommended to arrange group connection as shown in Figure 8.

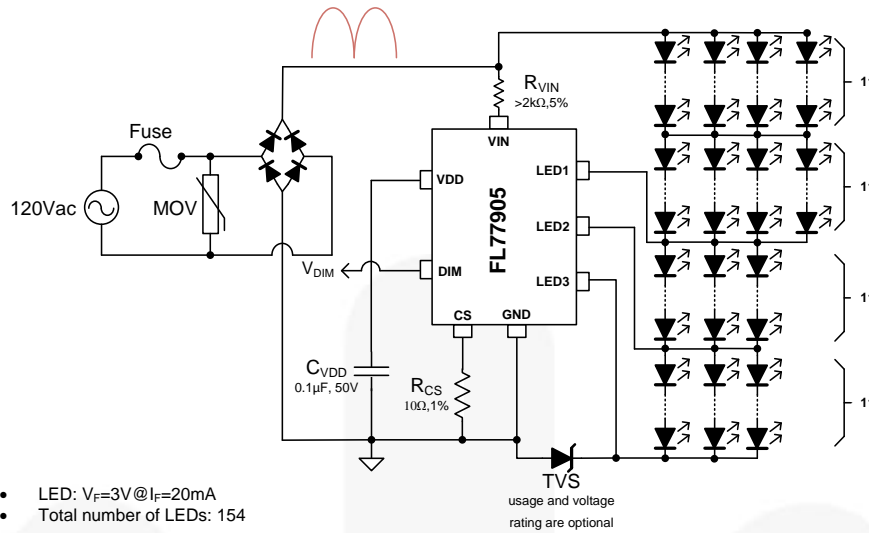


**Figure 6. 120-V<sub>AC</sub>, 8-W LED Configuration Having Different Number of Parallel LED Strings for Light Balancing**

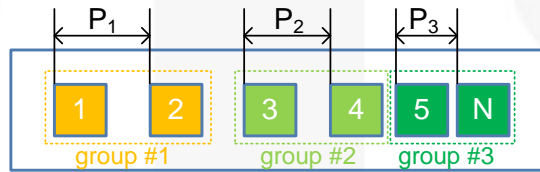

$$P_1:P_2:P_3 := I_{F1.AVG}:I_{F2.AVG}:I_{F3.AVG}$$

In design example,  $I_{F1.AVG}:I_{F2.AVG}:I_{F3.AVG} = 1.80:1.58:1$

**Figure 7. Spacing LEDs Based on Normalized Current Ratio**

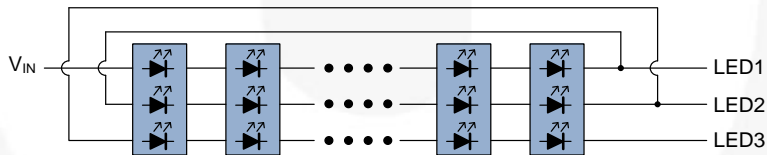

**Figure 8. LED Configuration for Tube Type Lighting Design using 3X LEDs**

## DIM Configuration

The FL77905 uses the DIM pin for analog, 0 V to 10 V, or pulse width modulation (PWM) dimming by applying a certain voltage which is below 5 V or PWM signals with 5 V peaks to the DIM pin. The LED channel sink and total RMS current through LEDs will be linearly changed with the  $V_{DIM}$  level, as shown in Figure 10 and Figure 11.

FL77905's DIM-pin function cannot be disabled. If DIM-pin function is not required, choose FL77904 instead. FL77904 can also be configured to use just three current regulators as in FL77905. Note that when DIM pin is floated, there will be no LED driving current as  $V_{DIM}=0$  since DIM pin does not source voltage by itself.

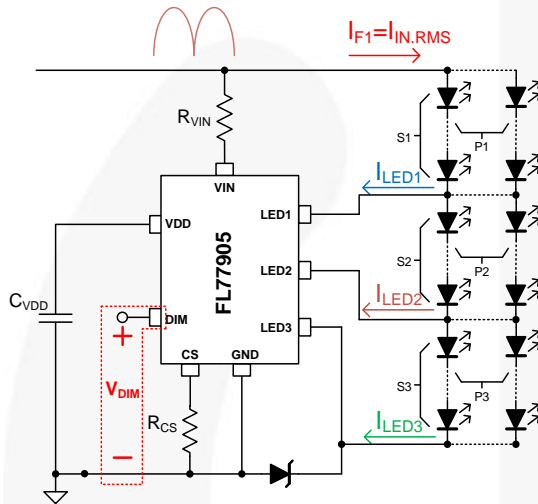


Figure 9. Analog or PWM Dimming

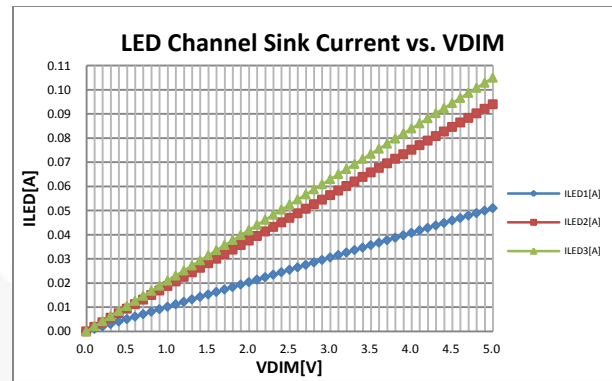


Figure 10. Regulated Current of Each Channel vs.  $V_{DIM}$  ( $R_{CS}=10\ \Omega$ )

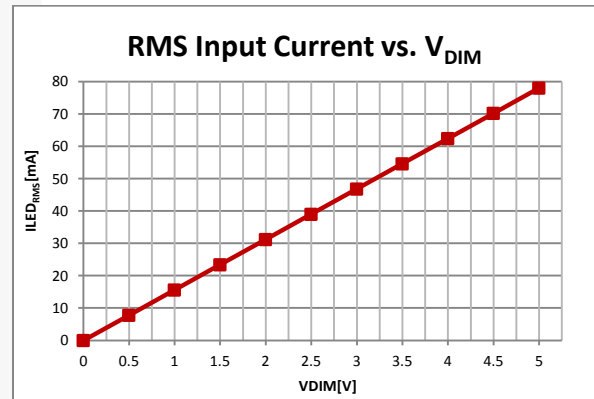


Figure 11. Input Current vs.  $V_{DIM}$  ( $R_{CS}=10\ \Omega$ )



## References

- [1] [\*“AN-5088 Designing for High Performance Commercial and Industrial Lighting Solution Using FL77944 High Power LED Direct AC Driver,” Fairchild Semiconductor, July 2016.\*](#)

## Related Datasheets

[\*FL77905 Analog / PWM / Phase-cut Dimmable Compact LED Direct AC Driver Datasheet\*](#)

---

### DISCLAIMER

FAIRCHILD SEMICONDUCTOR RESERVES THE RIGHT TO MAKE CHANGES WITHOUT FURTHER NOTICE TO ANY PRODUCTS HEREIN TO IMPROVE RELIABILITY, FUNCTION, OR DESIGN. FAIRCHILD DOES NOT ASSUME ANY LIABILITY ARISING OUT OF THE APPLICATION OR USE OF ANY PRODUCT OR CIRCUIT DESCRIBED HEREIN; NEITHER DOES IT CONVEY ANY LICENSE UNDER ITS PATENT RIGHTS, NOR THE RIGHTS OF OTHERS.

### LIFE SUPPORT POLICY

FAIRCHILD'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF FAIRCHILD SEMICONDUCTOR CORPORATION.

As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, or (c) whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

ON Semiconductor and  are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

## PUBLICATION ORDERING INFORMATION

### LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor  
19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA  
**Phone:** 303-675-2175 or 800-344-3860 Toll Free USA/Canada  
**Fax:** 303-675-2176 or 800-344-3867 Toll Free USA/Canada  
**Email:** [orderlit@onsemi.com](mailto:orderlit@onsemi.com)

**N. American Technical Support:** 800-282-9855 Toll Free  
USA/Canada  
**Europe, Middle East and Africa Technical Support:**  
Phone: 421 33 790 2910  
**Japan Customer Focus Center**  
Phone: 81-3-5817-1050

**ON Semiconductor Website:** [www.onsemi.com](http://www.onsemi.com)  
**Order Literature:** <http://www.onsemi.com/orderlit>  
For additional information, please contact your local  
Sales Representative