

Good Practice for the NCP1602 CSZCD Pin Design and PCB Layout

NCP1602 combines the current sense (CS) and the core demagnetization detection (ZCD, zero crossing detection) signals into a single pin named CSZCD. In some noisy environment, a non-optimum choice of sensing resistors combined with a dense PCB layout can lead to an unstable operation of 1602. This application note describes good practices for designing the circuitry around the NCP1602 CSZCD pin, including choice of component values and PCB layout.

Drain Connection for CSZCD Pin (Sensitivity to PCB Parasitics)

When trying to reduce the no-switching standby consumption current by increasing (above 1 MΩ) the resistance ($R_{CS1} + R_{CS2}$) of the CSZCD bridge connected between the drain and the source of the power MOSFET (see Figure 1), the sensitivity of the CSZCD pin to PCB parasitic capacitors is increased. In some case, it can lead to non-functionality caused for example by a constant false triggering of OCP (Over Current Protection) or OVP (Over Voltage Protection). This is due to the fact that the CSZCD voltage is distorted and the internal circuitry cannot work as intended. While recommendations for avoiding such CSZCD pin sensitivity are given in [1], this application note will focus only on optimizing the CSZCD pin operations.

 


Figure 1. The CSZCD Connection without an Auxiliary Winding

For safety and reliability reasons, the R_{CS1} resistor is generally made with three resistors in series ($R_{CS1,a}$, $R_{CS1,b}$ and $R_{CS1,c}$) shown in Figure 2.



ON Semiconductor®

www.onsemi.com

APPLICATION NOTE

Safety:

If one resistor gets shorted, the drain voltage which is high (e.g., 400 V) is not directly applied to CSZCD pin and no damage will be observed.

Reliability:

If $R_{CS1,a}$, $R_{CS1,b}$ and $R_{CS1,c}$ have the same resistance value, the power MOSFET drain voltage is divided by the resistors and each $R_{CS1,i}$ resistor has roughly one third of drain voltage across it, well under the max voltage rating of each resistor.

 


Figure 2. CSZCD Pin Circuitry Showing How R_{CS1} is Made

What are not shown in Figure 2 are the PCB parasitic capacitors C_{pi} and the CSZCD pin to GND parasitic capacitance $C_{CSZCDpar}$ which are shown in Figure 3. The parasitic capacitors C_{p0} and C_{p7} do not cause problems because C_{p0} together with the resistance R_{SENSE} create a very high frequency pole (well above the MHz range) and the same for V_{DRAIN} output impedance and C_{p7} .

On the contrary, when $R_{CS1,a}$, $R_{CS1,b}$ and $R_{CS1,c}$ values are getting close to $1\text{ M}\Omega$, very small parasitic capacitance values like for example 159 fF (femto farad) can create a pole at 1 MHz which is right in the range of the ringing frequency of power MOSFET drain voltage. As we want a distortion-free drain voltage image at the CSZCD pin, we are in trouble.

There is an internal zero inside the controller for cancelling the effect of the pole made by R_{CS} resistors and the CSZCD pin to grounds parasitic capacitor (mostly due to the TSOP6 package) $C_{CSZCDpar}$. In case C_{pi} have a low effect (C_{pi} values low and/or R_{CSi} values low), R_{CS} values are determined by the following Equations 1, 2 and 3.

$$R_{CS2} \geq 20\text{ k}\Omega \quad (\text{eq. 1})$$

$$\frac{R_{CS2} + R_{CS1,a} + R_{CS1,b} + R_{CS1,c}}{R_{CS2}} = 138 \pm 10\% \quad (\text{eq. 2})$$

$$\left[R_{CS0} + \frac{1}{\frac{1}{R_{CS2}} + \frac{1}{R_{CS1,a} + R_{CS1,b} + R_{CS1,c}}} \right] \cdot C_{CSZCDpar} \quad (\text{eq. 3})$$

$$= 500\text{ ns}$$

 


Figure 3. CSZCD Pin External Circuitry Showing Some of the PCB Parasitic Capacitors

Unfortunately, it is not possible to cancel the effects of MHz-range poles and zeroes created by the combination of PCB parasitic capacitances C_{pi} (there are even more C_{pi} than those shown in Figure 3, for example those coupling each node of the R_{CS} resistor ladder and DRV signal, V_{IN} signal, ...) by a schematic trick, and the only way to avoid problems is to keep C_{pi} values as low as possible and/or avoid $R_{CS1,a}$, $R_{CS1,b}$ and $R_{CS1,c}$ to have a value greater than $333\text{-k}\Omega$ ($R_{CS1,a} + R_{CS1,b} + R_{CS1,c}$ lower than $1\text{-M}\Omega$ limit).

While application note [1] already contains information, it is good to remind the following.

Do Not Do This

Using $R_{CS1,a} = R_{CS1,b} = R_{CS1,c}$ with $R_{CS1} = R_{CS1,a} + R_{CS1,b} + R_{CS1,c}$ if R_{CS1} is greater than $1\text{ M}\Omega$.

($R_{CS1} + R_{CS2}$) Lower than $1\text{ M}\Omega$

Three R_{CS1} 200-V SMD1206 resistors can be placed in series $R_{CS1} = R_{CS1,a} + R_{CS1,b} + R_{CS1,c}$.

($R_{CS1} + R_{CS2}$) Greater than $1\text{ M}\Omega$ and Lower than $5.12\text{ M}\Omega$

Bench experiments have shown that three SMD 200-V resistors of same value in series ($R_{CS1} = R_{CS1,a} + R_{CS1,b} + R_{CS1,c}$) lead to false fault tripping (e.g., OVP2 false triggering). It is advised to have one 500-V SMD high-value resistor $R_{CS1,c}$ on the drain side (e.g., $5.1\text{ M}\Omega$ for The EVB) with two low value (e.g., $240\text{ k}\Omega$) 200-V SMD resistors in series ($R_{CS1,a} + R_{CS1,b}$). This is to avoid having inter-resistor capacitance to GND and observe difficulties to discharge them before a t_{ON} cycle.

AND9454/D

Type of R_{CS} Resistors

Bench experiments have proven SMD1206 & 0805 superiority, parasitic capacitance wise, over through-hole resistors for R_{CS1} , R_{CS2} and R_{CS0} resistors.

PCB Layout Considerations

R_{CS0} must be placed as close as possible to CS/ZCD pin voltage and R_{CS1} and R_{CS2} as close as possible to R_{CS0} .

PCB traces connecting the R_{CSi} resistors must be kept as short as possible, the width of the trace being as small as possible (minimum parasitic capacitance).

It is wise to keep a safety distance of 1 cm between the high value resistors of the CSZCD bridge and DRV, V_{IN} , V_{DRAIN} copper traces to avoid coupling.

Showing Bad CSZCD Waveforms

As said before, very low parasitic capacitances between the nodes of the CSZCD divider bridge and GND creates a distorted CSZCD signal as shown in Figure 4 from both simulation and measurements. At the beginning of on-time, a voltage bump is added with can trigger OVS or OCP protections and during dead-time the parasitic capacitors are masking the image of drain voltage ringing which is well seen when the parasitic capacitances are low (see blue simulated curve on Figure 4)

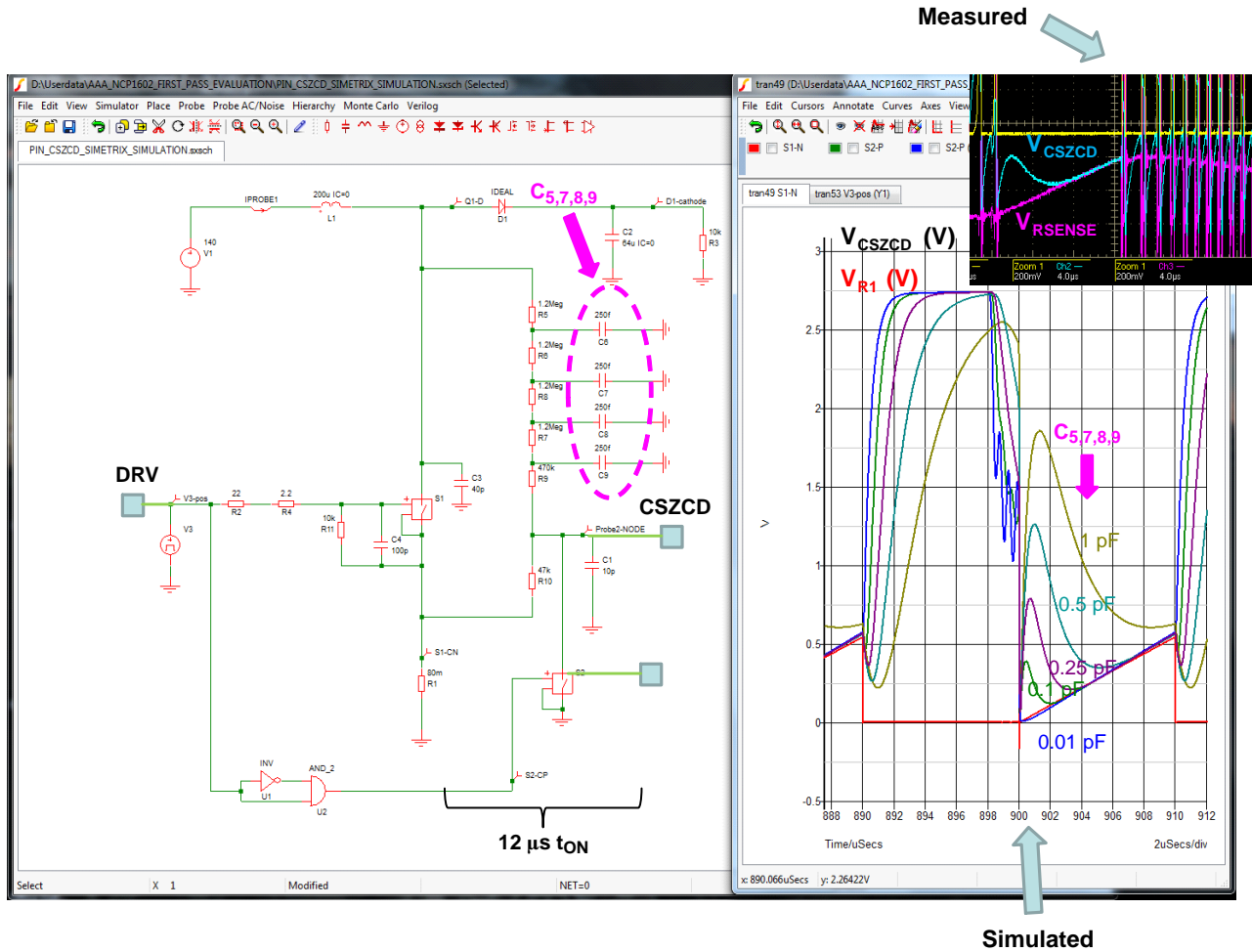



Figure 4. Effect of Parasitic Capacitances on CSZCD Signal

References

- [1] Application Note AND9218/D “5 Key Steps to Designing a Compact, High-Efficiency PFC Stage Using the NCP1602” which can be downloaded at: http://www.onsemi.com/pub_link/Collateral/AND9218-D.PDF

ON Semiconductor and  are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor
19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
USA/Canada
Europe, Middle East and Africa Technical Support:
Phone: 421 33 790 2910
Japan Customer Focus Center
Phone: 81-3-5817-1050

ON Semiconductor Website: www.onsemi.com
Order Literature: <http://www.onsemi.com/orderlit>
For additional information, please contact your local
Sales Representative