

AND9459/D

AM Radio Amplifier with Filter using the NSVJ3910SB3



ON Semiconductor®

www.onsemi.com

Overview

This application note explains about ON Semiconductor's NSVJ3910SB3 which is used as a Low Noise Amplifier (LNA) for AM Radio.

The NSVJ3910SB3 is a silicon junction field effect transistor best suited for high-frequency applications which is assembled in the 3-pin surface mount package.

For information about the performance, please refer to the datasheet of this product.

The evaluation board is adjusted to provide +9.5dB gain in AM band (520 to 1720 kHz) and reduce gain to -80dB in FM band (76 to 108 MHz).

A standard material FR4 is used for the printed circuit board (PCB).

APPLICATION NOTE

AND9459/D


■ Summary of Data

Ta = 25°C, Input Power = -40 dBm, Zo = 50 Ω


Parameter	Symbol	Condition	Result	Unit
DC Voltage	Vdd		5.0	V
DC Current	Idd		26.5	mA
Power Gain	Gp1	f = 520 kHz	9.45	dB
		f = 1120 kHz	9.85	
		f = 1720 kHz	9.81	
	Gp2	f = 76 MHz	-89.9	
		f = 90 MHz	-87.6	
		f = 108 MHz	-82.3	
Input Return Loss	RLin	f = 520 kHz	-0.03	dB
		f = 1120 kHz	-0.19	
		f = 1720 kHz	-0.48	
Output Return Loss	RLout	f = 520 kHz	-0.81	dB
		f = 1120 kHz	-1.08	
		f = 1720 kHz	-1.67	
Isolation	ISL	f = 520 kHz	-48.2	dB
		f = 1120 kHz	-41.5	
		f = 1720 kHz	-37.9	

AND9459/D

■Circuit Design

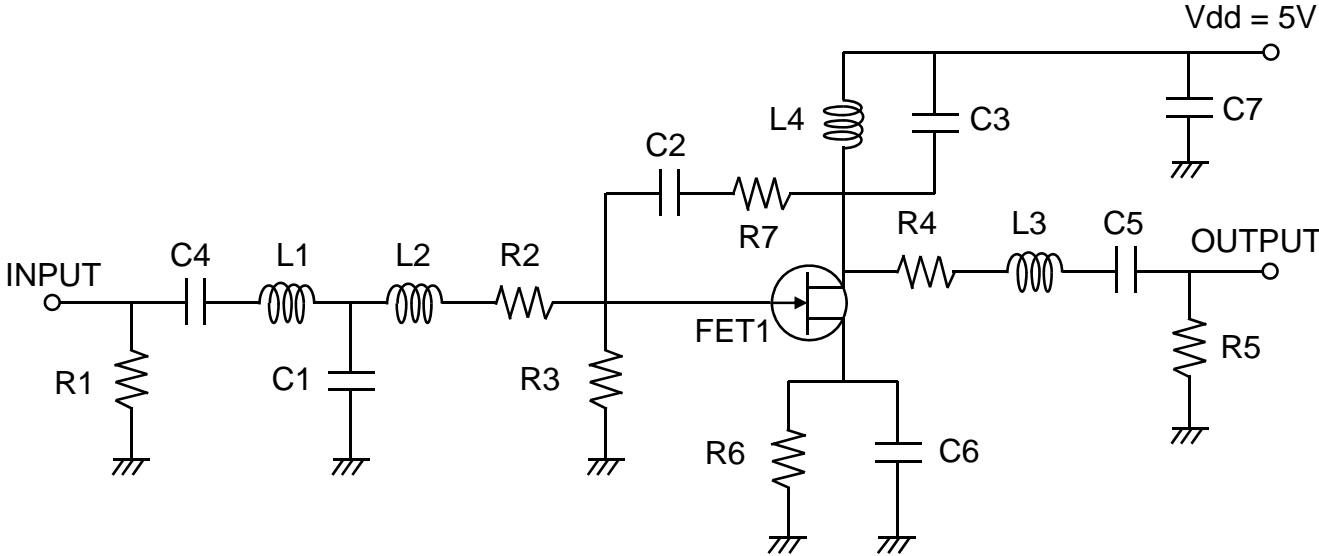

■Evaluation Board

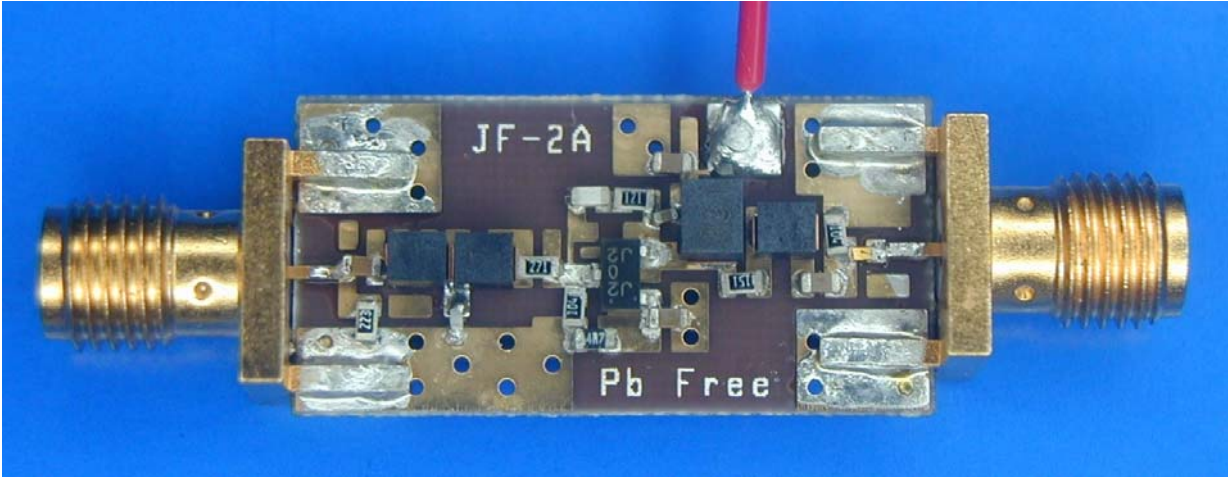

AND9459/D

■Bill of Materials

Item	Symbol	Value	Manufacture	Size
J-FET	FET1	NSVJ3910SB3	ON Semiconductor	SC-59
Capacitor	C1	10 pF	Murata GRM155	1005
	C2	12 pF	Murata GQM188	1608
	C3	120 pF	Murata GRM155	1005
	C4,C5,C6,C7	0.1 uF	ROHM MCH182CN	1608
Resistor	R1	22 k Ω	Various	1608
	R2	270 Ω	Various	1608
	R3	100 k Ω	Various	1608
	R4	150 Ω	Various	1608
	R5	100 k Ω	Various	1608
	R6	4.7 Ω	Various	1608
	R7	120 k Ω	Various	1608
Inductor	L1,L2,L3	3.3 uH	TDK NLV25T	2520
	L4	330 uH	TDK NLCV32T	3225
Material		FR-4		25 x 13 mm

■ Measurement Results

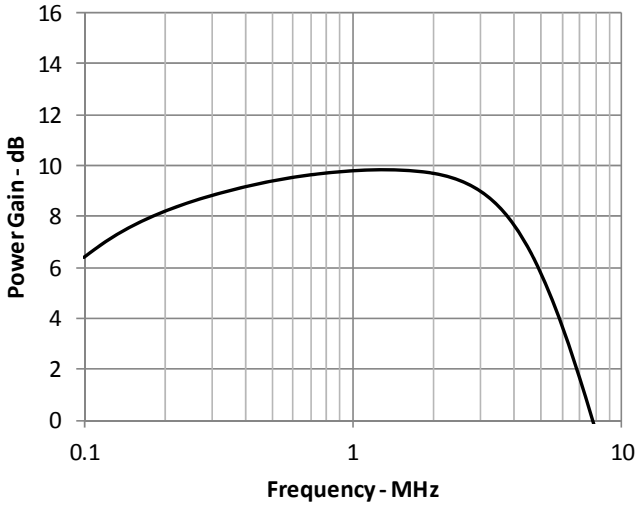


Figure 1 Power Gain vs. Frequency

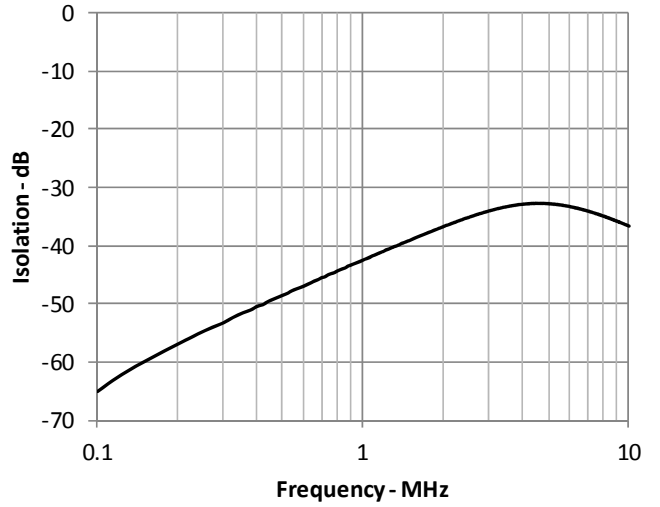


Figure 2 Isolation vs. Frequency

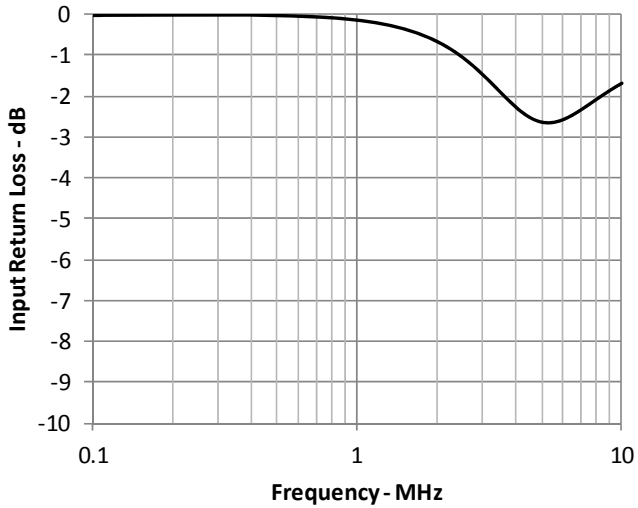


Figure 3 Input Return Loss vs. Frequency

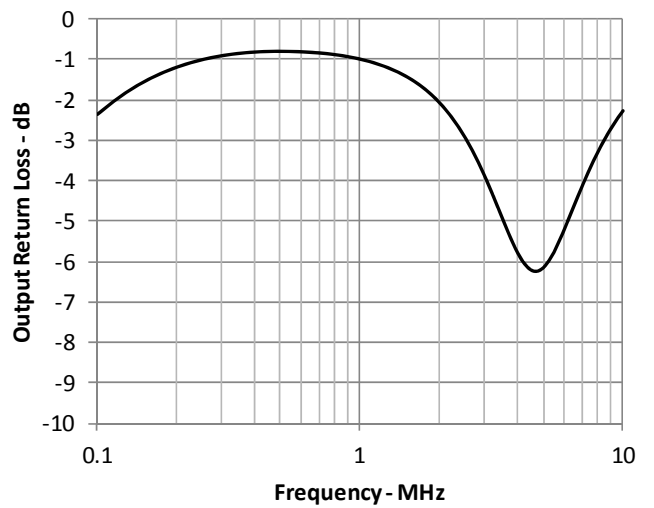


Figure 4 Output Return Loss vs. Frequency

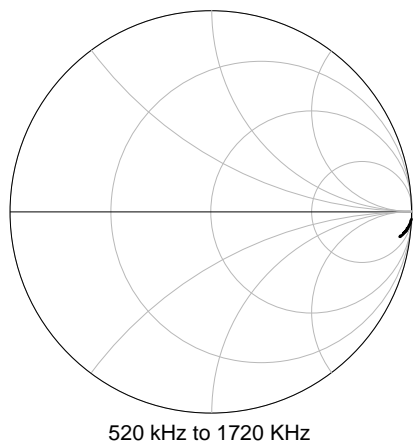


Figure 5 Smith Chart S11

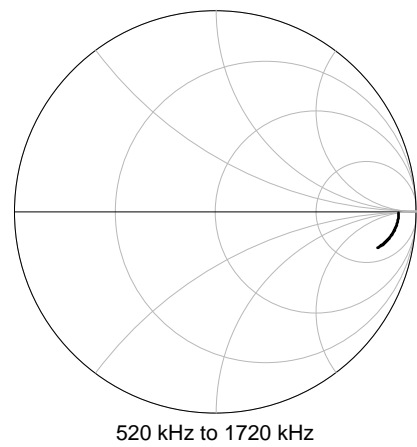


Figure 6 Smith Chart S22

■ Measurement Results

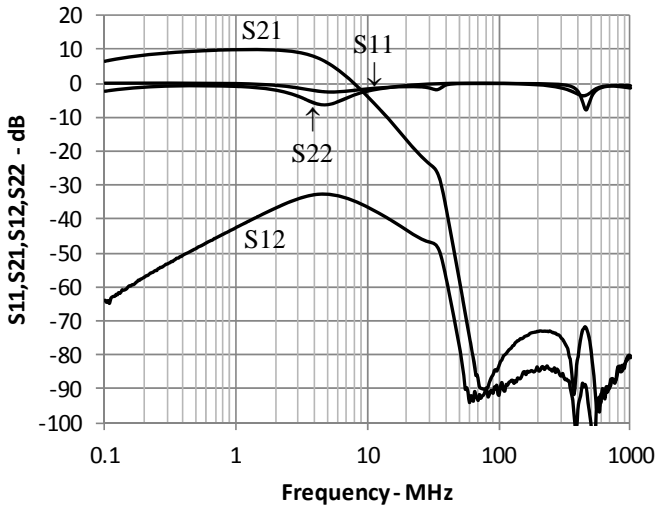


Figure 7 Wide Span

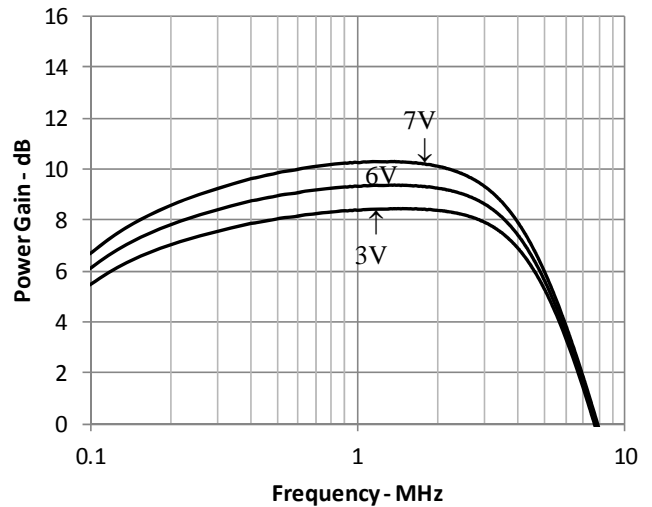


Figure 8 Voltage Dependency

ON Semiconductor and the ON Semiconductor logo are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.