

ON Semiconductor

Is Now

onsemi™

To learn more about onsemi™, please visit our website at
www.onsemi.com

onsemi and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.



NCP107X, 12 Vout, Off-line Buck Regulator

ON Semiconductor

Device	Application	Input Voltage	Output Power	Topology	I/O Isolation
NCP1071 NCP1075 NCP1077	Smart Meters Electric Meters, White Goods	85 to 265 Vac	Up to 6 W at 12 Vout	Off-Line 100 kHz Buck	Non-isolated

Output Specification	
Output Voltage	5 to 36 Vdc depending on selected Z1 zener value
Output Ripple	Less than 1%
Typical Current	100 to 350 mA
Max Current	150 mA with NCP1071, 400 mA with NCP1077 (see matrix below)
Min Current	zero

PFC (Yes/No)	No, Pout < 25 watts
Efficiency	See plots below
Inrush Limiting / Fuse	External fuse required
Operating Temp. Range	0 to +50°C (dependent on U1 heatsinking)
Cooling Method / Supply Orientation	Convection
Signal Level Control	None

Circuit Description

This design note describes a very simple, low power, constant voltage output buck power converter intended for powering electronics for white goods, electrical meters, and industrial equipment where isolation from the AC mains is not required. The switching element in the converter is ON Semiconductor's NCP107x series of monolithic switchers. In this reference design, the NCP1071 is utilized with a 100 kHz switching frequency and a maximum output current of 250 mA.

This buck circuit design utilizes a simple charge pump or "bootstrap" type of voltage sensing and regulation scheme composed of D4, C5, Z1, Q1 and the associated passive components. This simple sensing technique eliminates the use of an optocoupler in the feedback loop. Z1 sets the approximate output voltage and Q1 acts as a simple error amplifier. Although the regulation is inferior to that of a conventional TL431 and optocoupler feedback circuit, it is typically adequate for most applications with a regulation of +/- 5% over loads from 100%

down to about 1% max rated load. Below 1% the output will rise to the value of the overvoltage clamping zener Z2 across the output. For a 12 volt output, a typical value for this zener will be 15 volts and at no load, the output will be clamped at this level.


The sensed voltage produced on C5 is also used to power the NCP1071 controller through D2 and limiting resistor R1 once the converter has started. This auxiliary Vcc to run the chip improves the overall efficiency of the circuit and prevents the controller from running in DSS mode under normal load conditions.

Because of the low power output, a simple half-wave input rectifier/filter circuit is used comprised of D1 and C2. C1 and L1 form a conducted EMI filter that easily meets CE and UL level B requirements. C2 can be reduced to 1/2 the specified capacitance if a full-wave bridge rectifier circuit is used on the input.

The 1.5 mH buck output inductor is available in several surface mount configurations from multiple vendors.

DN05058/D

Schematic

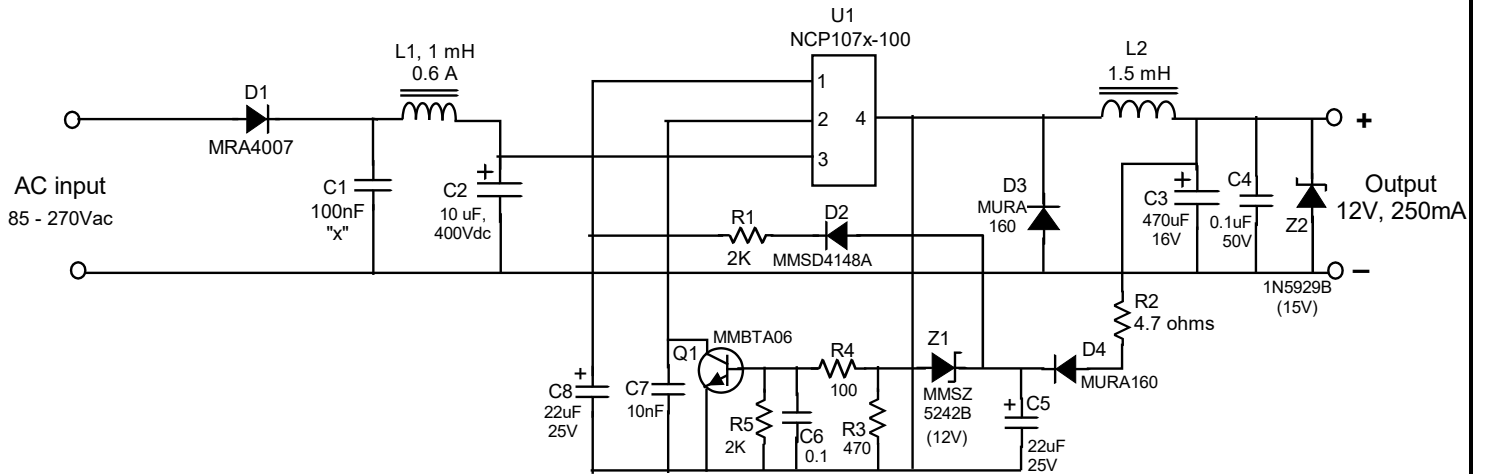


Notes:


1. Vout set by Z1 ($V_{out} = V_z + 0.5V$ approx - adjust with R5).
2. L1 is Würth 744732102.
3. Z2 is optional output OVP zener (15V).
4. R1 sets Vcc max current to avoid OVP trip.
5. L2 is Würth 7687709152 (1.5 mH, 500 mA)
6. Crossed schematic lines are not connected.

Off-Line Buck Converter Using NCP1070
With Charge Pump Voltage Sensing (R4)


Output Regulation

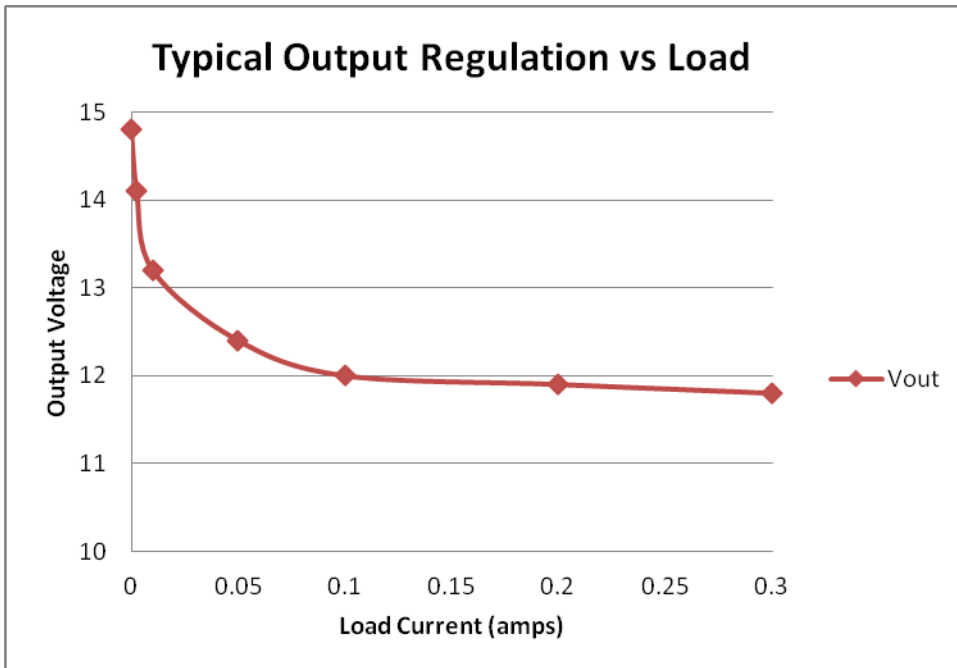

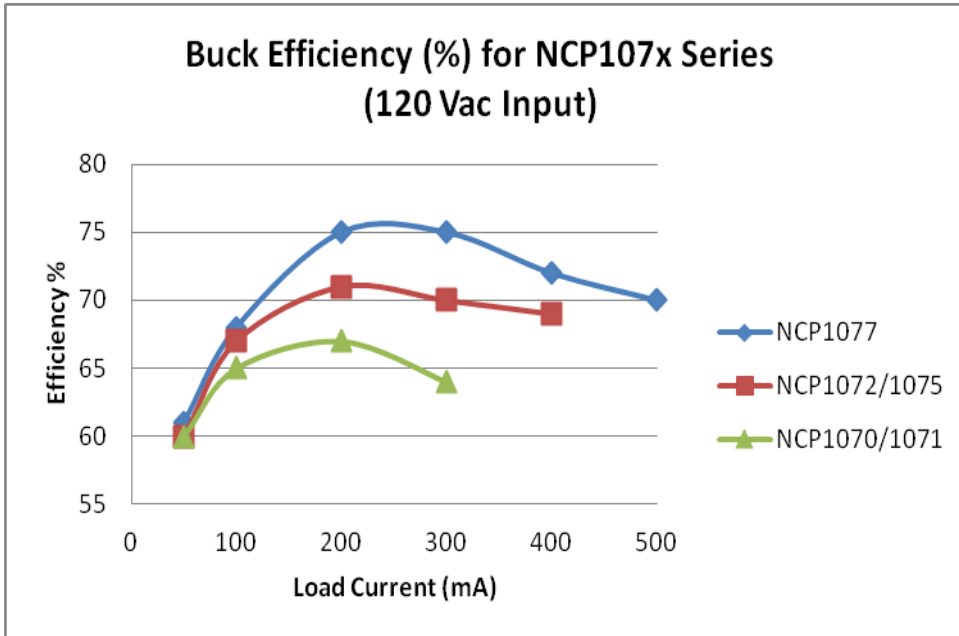
Typical Efficiency vs Load at 120 Vac Input for NCP107x Series



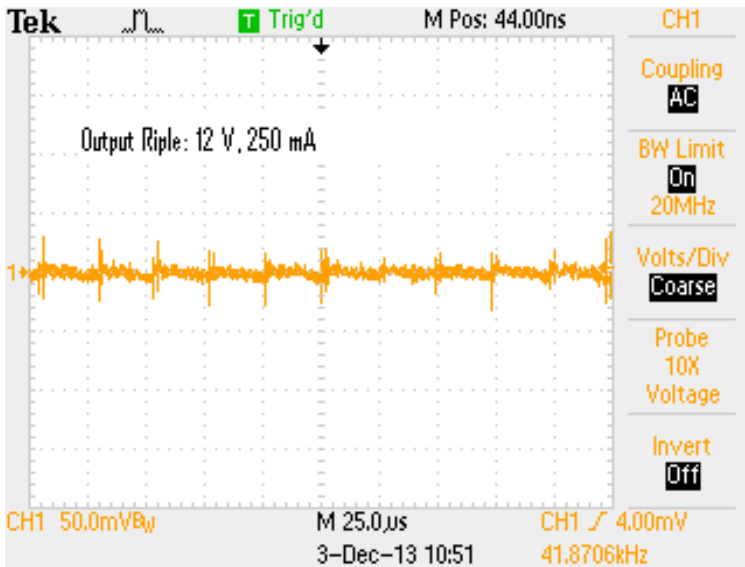Output Ripple – 250 mA Load, 120 Vac Input



Conducted EMI Profile (12Vout @ 250 mA)

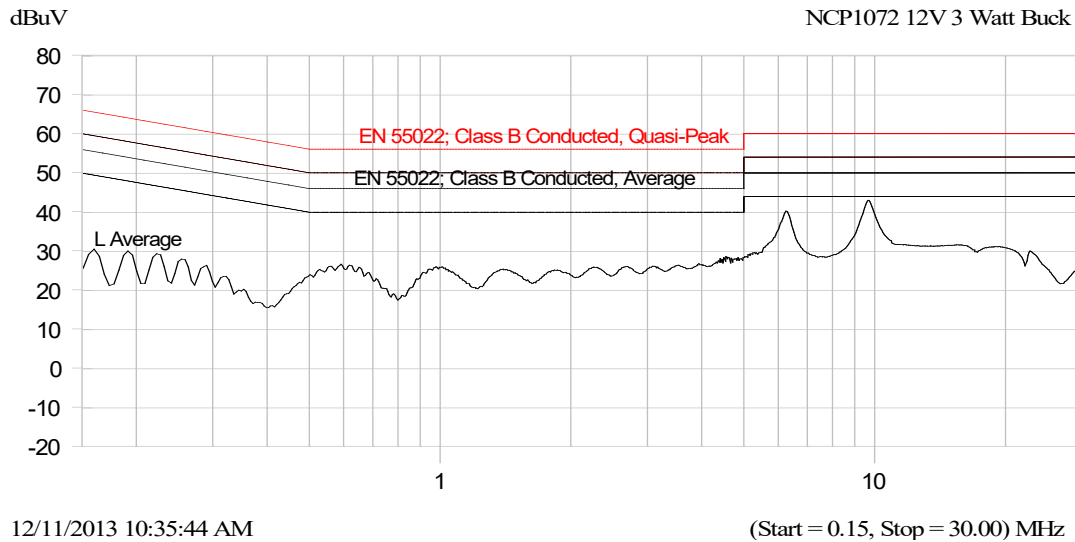

NCP107x Buck Converter Maximum Output Current Matrix

Part	Continuous Limit	Peak Transient Limit
NCP1070	100 mA	1500 mA
NCP1071	150 mA	200 mA
NCP1072	150 mA	200 mA
NCP1075	250 mA	300 mA
NCP1076	300 mA	350 mA
NCP1077	400 mA	500 mA

References:

ON Semiconductor Application Notes: AND8318, AND8328
 ON Semiconductor Design Notes: DN05014, DN05023, DN5053, DN06011, DN06052
 ON Semiconductor NCP1070, NCP1075 and NCP1077 monolithic switcher data sheets.

© 2013 ON Semiconductor.

Disclaimer: ON Semiconductor is providing this design note "AS IS" and does not assume any liability arising from its use; nor does ON Semiconductor convey any license to its or any third party's intellectual property rights. This document is provided only to assist customers in evaluation of the referenced circuit implementation and the recipient assumes all liability and risk associated with its use, including, but not limited to, compliance with all regulatory standards. ON Semiconductor may change any of its products at any time, without notice.

Design note created by Frank Cathell, e-mail: f.cathell@onsemi.co

